Circuit diagram: Left branch shows current i_{in} flowing into a resistor labeled $\frac{1}{g_m}$. Right branch shows current i_{out} with a dependent current source labeled $-i_{in}$ and a resistor labeled $R_D || (r_o + g_m r_o R_s)$.